

UNIT 5 - CHAPTER 9

DC MACHINE

9.1 ELECTRO MECHANICAL ENERGY CONVERSION (EMEC)

According to electro mechanical energy conversion “Electrical energy can be converted in to mechanical energy or mechanical energy can be converted in to electrical energy”.

EMEC based on the principle of energy conservation.

According to energy conservation “Energy can neither be created nor be destroyed only we can convert the energy from one form to other form”.

For converting the electrical energy and mechanical energy to each other we have to connect both the energy with the help of a field called coupling field. Two types of field are available to connect both the energy namely

- (1) Electric field
- (2) Magnetic field

The field which we use to connect the energy is magnetic field. As shown in fig. 9.1.

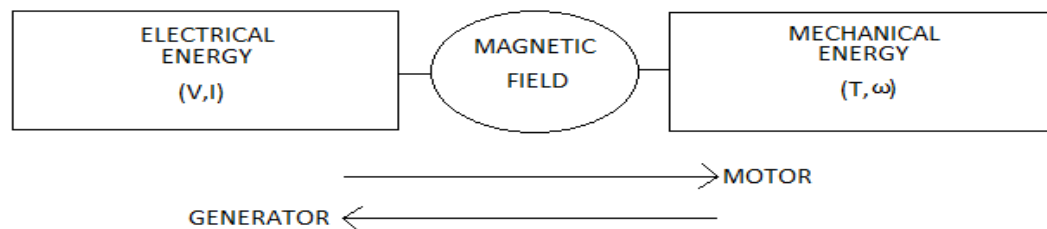


Fig. 9.1

Motor: The machines which convert electrical energy into mechanical energy is called motor. We have to supply input of voltage (V) and current (I) to motor and motor will give us torque (T) and angular speed (ω) as output.

Generator: The machines which convert mechanical energy into electrical energy is called generator. We have to supply input of torque (T) and angular speed (ω) to generator and generator will give us voltage (V) and current (I) as output.

9.2 CLASSIFICATION OF ELECTRICAL MACHINE

We are having two types of electrical supply so electrical machine are of two types as shown in fig. 9.2.

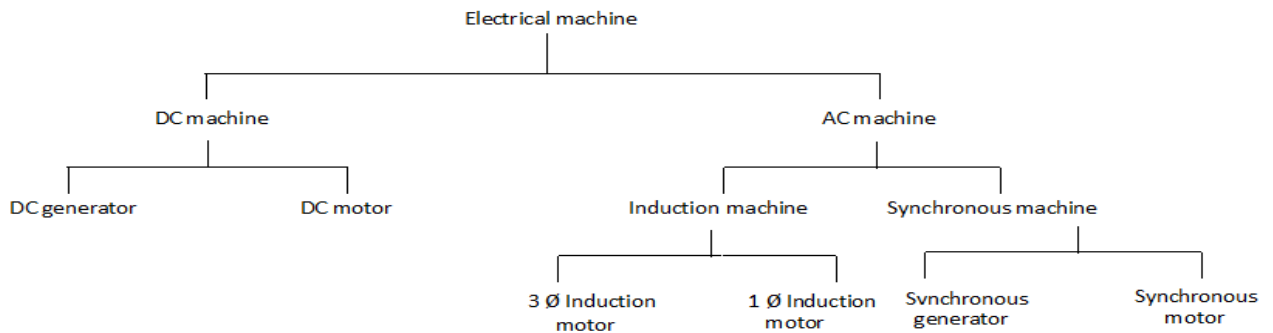


Fig. 9.2

9.3 CONSTRUCTION OF DC MACHINE

Construction of DC machine is same whether it is generator or motor. The construction of DC machine consist of the following parts is shown in fig. 9.3.

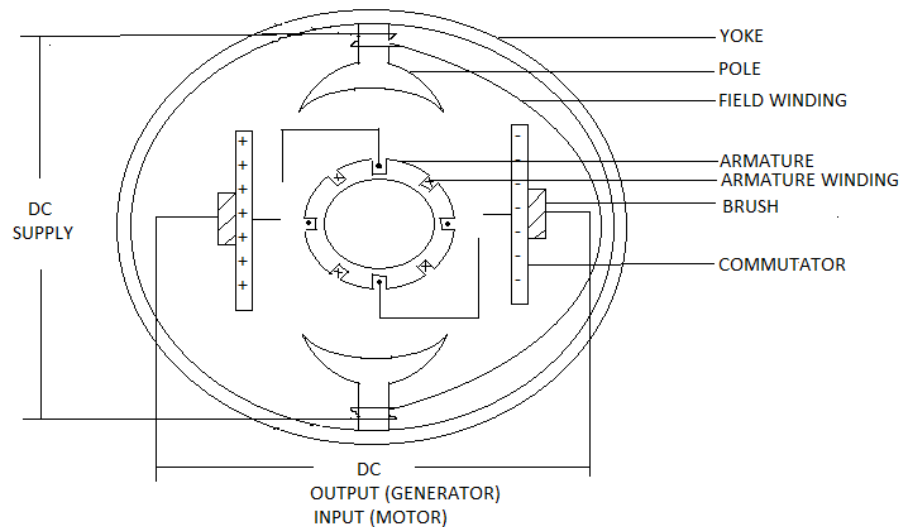


Fig. 9.3

- (1) Yoke: It is the outer cover of the DC machine. The poles of the DC machine are fixed on the yoke. The yoke serve the following two functions.
 - (i) It provides the mechanical support to the machine.
 - (ii) It save the winding from the dust, water etc.
- (2) Field system: It is the stationary part of the DC machine. The purpose of the field system is to provide the coupling magnetic field. The field system of the DC machine consist the poles and field winding. When DC supply is provided to the field winding the magnetic field is produce between the poles.
- (3) Armature: It is the rotating part of the DC machine. The purpose of the armature is to rotate the armature winding in the magnetic field. The shape of the armature is cylindrical and it consist the slot on its outer surface. The conductor are placed in these slots and known as armature winding. A small air gap exists between the poles and armature. Armature winding are basically of two types.

Induced emf by one conductor in one revolution

$$\frac{\text{Generated emf}}{\text{conductor}} = \frac{P\phi}{60/N} = \frac{P\phi N}{60}$$

Total generated emf

$$\begin{aligned} E_g &= \text{emf per parallel path} \\ &= \left(\frac{\text{Generated emf}}{\text{conductor}} \right) \times \text{Number of conductor in per parallel path} \\ &= \frac{P\phi N}{60} \times \frac{Z}{A} \\ E_g &= \frac{P\phi NZ}{60A} \end{aligned}$$

For LAP winding $A = P$

$$E_g = \frac{\phi NZ}{60}$$

For WAVE winding $A = 2$

$$E_g = \frac{P\phi NZ}{120}$$

9.6 DC MOTOR

The DC motor is machines which convert DC electrical energy into mechanical energy.

Principle: The DC motor work on the principle of “When a current carrying conductor is placed in the magnetic field, then conductor experience a force and conductor will rotate”.

Working: The working of the DC motor is as follow.

- (1) The DC supply is given to the field winding, so a uniform magnetic flux is setup.
- (2) A DC electrical energy is provided to the armature, commutator convert this DC into AC and supply this AC to the armature winding.
- (3) Now armature winding is current carrying conductor and placed in the magnetic field, so armature winding experience a force and armature winding will rotate.
- (4) The armature winding is connected on the armature so with the armature winding, armature will also rotate.
- (5) So the DC electrical energy given to the armature is converted in to mechanical energy.

9.7 BACK EMF IN THE DC MOTOR

When the armature winding of the motor rotates, the armature winding cut the magnetic flux. Therefore an EMF is induced in the armature winding. This EMF is known as back EMF because this RMF always opposes the supply voltage. The expression for the back EMF is

$$E_b = \frac{P\phi NZ}{60A}$$

Importance: The presence of back emf makes the DC motor a self- regulating machine. It makes the DC motor to draw as much armature current which is sufficient to produce the required torque.

9.8 TORQUE EQUATION OF THE DC MOTOR

Let

$$T_a = \text{Armature torque}$$

E_b = Back emf

I_a = Armature current

N = Motor speed in rpm

ω = Angular speed

Electrical power in the armature = $E_b I_a$

Mechanical power developed by the armature = $T_a \omega = T_a \frac{2\pi N}{60}$

The electrical power in the armature is converted in to the mechanical power so

Electrical power in the armature = Mechanical power developed by the armature

$$E_b I_a = T_a \frac{2\pi N}{60}$$

We know

$$E_b = \frac{P\phi NZ}{60A}$$

So

$$\frac{P\phi NZ}{60A} I_a = T_a \frac{2\pi N}{60}$$

$$T_a = \frac{1}{2\pi} \frac{P\phi Z I_a}{A}$$

$$T_a = 0.159 \frac{P\phi Z I_a}{A}$$

The P , Z , A are constant, so

$$T_a \propto \phi I_a$$

Torque is proportional to the flux ϕ and Armature current I_a

For DC series motor

$$\phi \propto I_a \quad \text{so} \quad T_a \propto I_a^2$$

For DC shunt motor

$$\phi \propto \text{constant} \quad \text{so} \quad T_a \propto I_a$$

9.9 CHARACTERISTIC OF DC MOTOR

The characteristic of the DC motor are the graph between the different quantities.

9.9.1 **Torque and Armature current characteristic (T/I_a):** It is the graph between the Torque (T) and Armature current (I_a).



DC series

DC shunt

We know

$$T_a \propto I_a^2$$

$$T_a \propto I_a$$

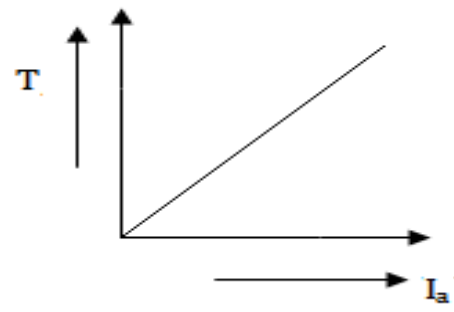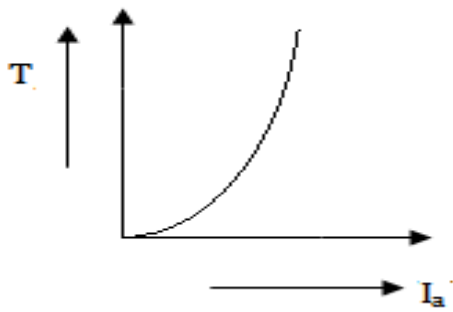

9.9.2 **Speed and Armature current characteristic (N/I_a):** It is the graph between the Speed (N) and Armature current (I_a).



DC series

DC shunt

We know

$$N \propto \frac{1}{I_a}$$

$$N \propto \text{constant}$$

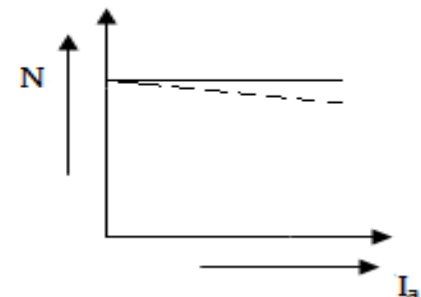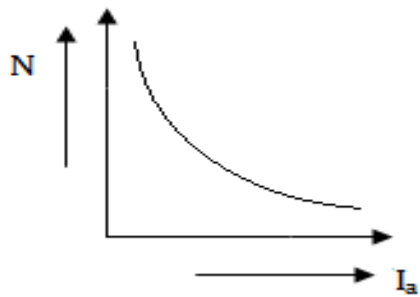

9.9.3 **Speed and Torque characteristic (N/T):** It is the graph between the Speed (N) and Torque (T).



DC series

DC shunt

We know

$$N \propto \frac{1}{T}$$

$$N \propto \text{constant}$$

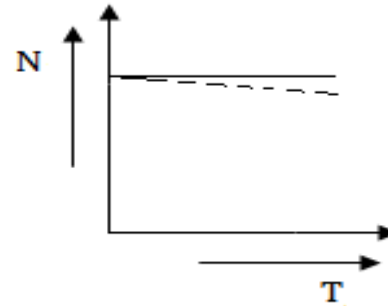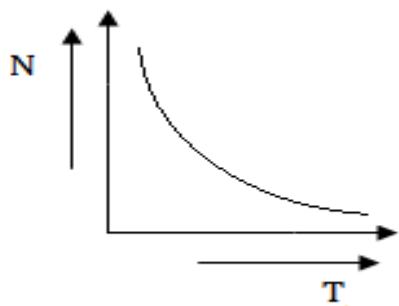

9.10 TYPES OF THE DC MACHINE

The field winding and armature winding are connected to each other. They are connected either in series or parallel, so DC machines are of two types

9.10.1 **DC series machine:** In DC series machine field and armature winding are connected in series. The DC series generator and DC series motor is shown in fig. 9.4 (a) and 9.4 (b) respectively. In the case of generator the direction of current is outward and in the case of motor the direction of current is inward.

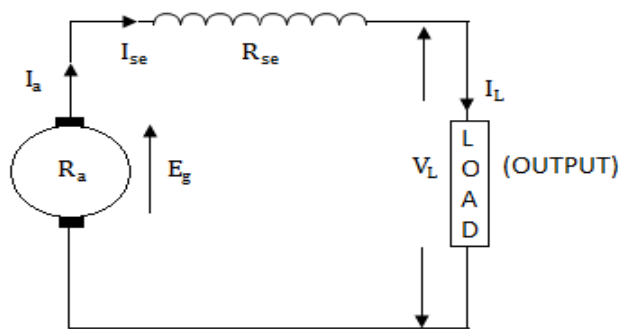


Fig. 9.4 (a)

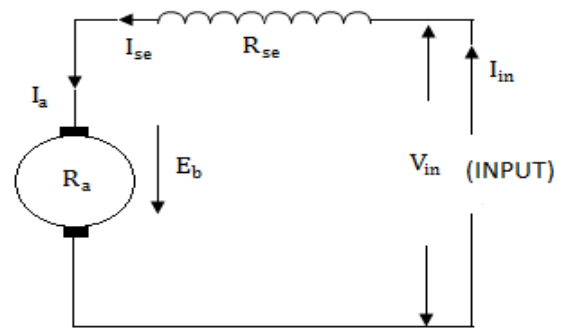


Fig. 9.4 (b)

Where

R_a = Armature resistance

I_a = Armature current

E_g = Generated emf

I_{se} = Series field winding current

R_{se} = Series field winding resistance

V_L = Load voltage (Output voltage)

I_L = Load current (Output current)

Current equation

$$I_a = I_{se} = I_L$$

Voltage equation

$$E_g = I_a R_a + I_{se} R_{se} + V_L$$

Electrical power develop in armature

$$P_a = E_g I_a$$

Power delivered to the load (Output power)

$$P_L = V_L I_L$$

Where

R_a = Armature resistance

I_a = Armature current

E_b = Back emf

I_{se} = Series field winding current

R_{se} = Series field winding resistance

V_{in} = Input voltage

I_{in} = Input current

Current equation

$$I_a = I_{se} = I_{in}$$

Voltage equation

$$V_{in} = I_{se} R_{se} + I_a R_a + E_b$$

Electrical power develop in armature

$$P_a = E_b I_a$$

Power input to the motor (Input power)

$$P_{in} = V_{in} I_{in}$$

9.10.2 **DC shunt machine:** In DC shunt machine field and armature winding are connected in parallel. The DC shunt generator and DC shunt motor is shown in fig. 9.5 (a) and 9.5 (b) respectively.

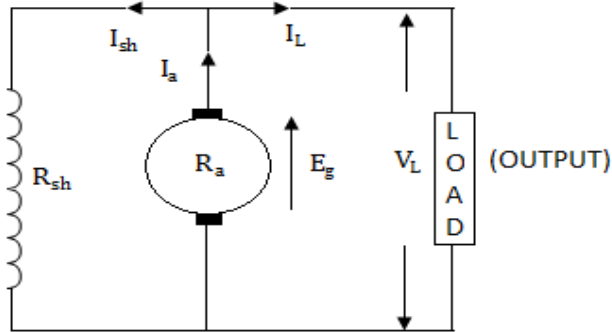


Fig. 9.5 (a)

Where

R_a = Armature resistance

I_a = Armature current

E_g = Generated emf

I_{sh} = Shunt field winding current

R_{sh} = Shunt field winding resistance

V_L = Load voltage (Output voltage)

I_L = Load current (Output current)

Current equation

$$I_a = I_{sh} + I_L$$

Voltage equation

$$E_g = I_a R_a + V_L$$

Electrical power develop in armature

$$P_a = E_g I_a$$

Power delivered to the load (Output power)

$$P_L = V_L I_L$$

Shunt field winding current

$$I_{sh} = \frac{V_L}{R_{sh}}$$

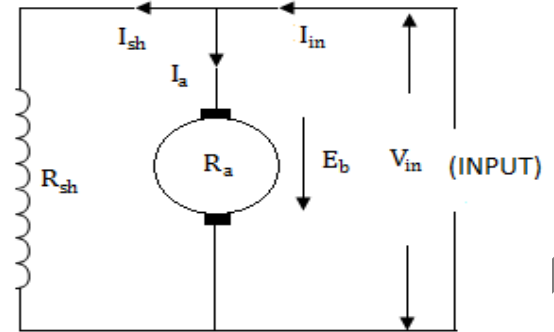


Fig. 9.5 (b)

Where

R_a = Armature resistance

I_a = Armature current

E_b = Back emf

I_{sh} = Shunt field winding current

R_{sh} = Shunt field winding resistance

V_{in} = Input voltage

I_{in} = Input current

Current equation

$$I_{in} = I_a + I_{sh}$$

Voltage equation

$$V_{in} = I_a R_a + E_b$$

Electrical power develop in armature

$$P_a = E_b I_a$$

Power input to the motor (Input power)

$$P_{in} = V_{in} I_{in}$$

Shunt field winding current

$$I_{sh} = \frac{V_{in}}{R_{sh}}$$

9.11 APPLICATION OF DC MOTOR


9.11.1 **Application of series motor:** (1) Cranes (2) Elevators (3) Trolleys (4) Conveyors (5) Hoists (6) Electric locomotives

9.11.2 **Application of shunt motor:** (1) Blowers (2) Centrifugal pump (3) Lathe machine (4) Milling machine (5) Drilling machine (6) Reciprocating machine

9.12 NUMERICAL OF DC MACHINE

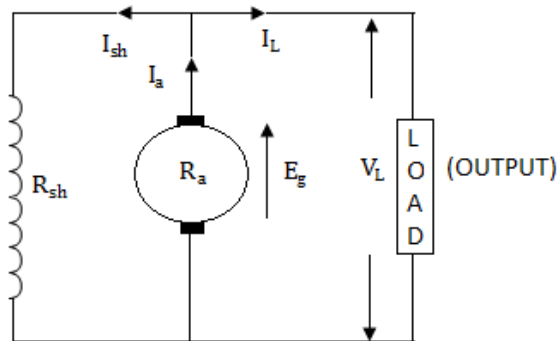Example 9.1 A 20 kW, 250 V DC shunt generator has an armature resistance of 0.04 Ω and a shunt field resistance of 250 Ω . Calculate the power developed in the armature and power delivered to the load.

Solution: Given $P_L = 20 \text{ kW}$, $V_L = 250 \text{ V}$, $R_a = 0.04 \Omega$, $R_{sh} = 250 \Omega$, DC SHUNT GENERATOR



We know

$$P_L = V_L I_L \Rightarrow I_L = \frac{P_L}{V_L} = \frac{20 \times 10^3}{250} = 80 \text{ Amp.}$$

Shunt field current

$$I_{sh} = \frac{V_L}{R_{sh}} = \frac{250}{250} = 1 \text{ Amp.}$$

From the current equation

$$I_a = I_{sh} + I_L = 1 + 80 = 81 \text{ Amp.}$$

From the voltage equation

$$E_g = I_a R_a + V_L = 81 \times 0.04 + 250 = 3.24 + 250 = 253.24 \text{ V}$$

Power developed in the armature


$$P_a = E_g I_a = 253.24 \times 81 = 20512.44 \text{ W} = 20.5124 \text{ kW Ans.}$$

Power delivered to the load

$$P_L = V_L I_L = 250 \times 80 = 20000 \text{ W} = 20 \text{ kW Ans.}$$

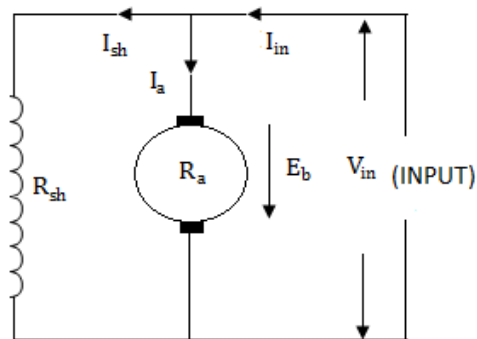Example 9.2 A 30 kW, 250 V DC shunt motor has an armature resistance of 0.04Ω and a shunt field resistance of 250Ω . Calculate the power developed in the armature and power input to the motor.

Solution: $P_{in} = 30 \text{ kW}$, $V_{in} = 250 \text{ V}$, $R_a = 0.04 \Omega$, $R_{sh} = 250 \Omega$, DC SHUNT MOTOR



We know

$$P_{in} = V_{in} I_{in} \Rightarrow I_{in} = \frac{P_{in}}{V_{in}} = \frac{30 \times 10^3}{250} = 120 \text{ Amp.}$$

Shunt field current

$$I_{sh} = \frac{V_{in}}{R_{sh}} = \frac{250}{250} = 1 \text{ Amp.}$$

From the current equation

$$I_{in} = I_a + I_{sh} \Rightarrow I_a = I_{in} - I_{sh} = 120 - 1 = 119 \text{ A}$$

From the voltage equation

$$V_{in} = I_a R_a + E_b \Rightarrow E_b = V_{in} - I_a R_a = 250 - 119 \times 0.04 = 245.24 \text{ V}$$

Power developed in the armature

$$P_a = E_b I_a = 245.24 \times 119 = 29183.56 \text{ W} = 29.183 \text{ kW Ans.}$$

Power delivered to the load


$$P_{in} = V_{in} I_{in} = 250 \times 120 = 30000 \text{ W} = 30 \text{ kW Ans.}$$

Example 9.3 A 4 – pole DC shunt generator armature has 40 slots each having 12 conductors. Armature resistance is 1Ω and shunt field resistance is 250Ω . The flux per pole is 25 mWb . If a load of 50Ω is

connected across the armature terminal. Calculate the voltage across the load when the generator is driven at 1000 rpm. What will be the load voltage if

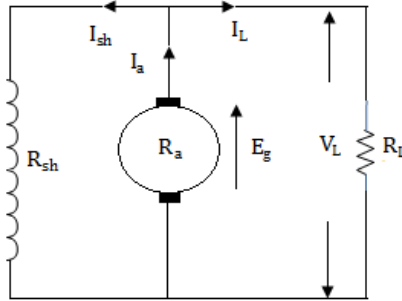- (1) Generator is Lap wound (2) Generator is wave wound

Solution: Given $P = 4$, $R_a = 1 \Omega$, $R_{sh} = 250 \Omega$, $Z = 40 \times 12 = 480$, $\phi = 25 \text{ mWB}$, $N = 1000 \text{ rpm}$, $R_L = 50 \Omega$, DC SHUNT GENERATOR



- (1) Generator is Lap wound

$$A = P = 4$$

$$E_g = \frac{P\phi NZ}{60A} = \frac{4 \times 25 \times 10^{-3} \times 1000 \times 480}{60 \times 4} = 200 \text{ V}$$

Load current

$$I_L = \frac{V_L}{R_L} = \frac{V_L}{50}$$

Shunt field current

$$I_{sh} = \frac{V_L}{R_{sh}} = \frac{V_L}{250}$$

From the current equation

$$I_a = I_{sh} + I_L = \frac{V_L}{250} + \frac{V_L}{50} = \frac{6V_L}{250}$$

From the voltage equation

$$E_g = I_a R_a + V_L$$

$$200 = \frac{6V_L}{250} \times 1 + V_L \Rightarrow V_L = \frac{200 \times 250}{256} = 195.3125 \text{ Ans.}$$

- (2) Generator is wave wound

$$A = 2$$

$$E_g = \frac{P\phi NZ}{60A} = \frac{4 \times 25 \times 10^{-3} \times 1000 \times 480}{60 \times 2} = 400 \text{ V}$$

Load current

$$I_L = \frac{V_L}{R_L} = \frac{V_L}{50}$$

Shunt field current

$$I_{sh} = \frac{V_L}{R_{sh}} = \frac{V_L}{250}$$

From the current equation

$$I_a = I_{sh} + I_L = \frac{V_L}{250} + \frac{V_L}{50} = \frac{6V_L}{250}$$


From the voltage equation

$$E_g = I_a R_a + V_L$$

$$400 = \frac{6V_L}{250} \times 1 + V_L \Rightarrow V_L = \frac{400 \times 250}{256} = 390.625 \text{ Ans.}$$

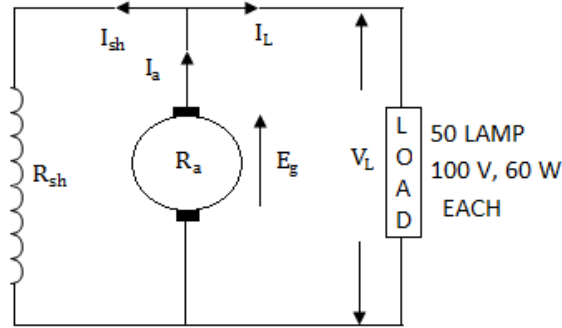Example 9.4 A 4 – pole Dc shunt generator with Lap connected armature has field and armature resistance of 100Ω and 0.2Ω respectively. It supplies power to 50 lamp rated for 100 V, 60 W each. Calculate the total armature current and the generated emf by allowing a contact drop of 1 V per brush.

Solution: Given $P = 4$, $A = P = 4$, $P_L = 50 \times 60 = 3000 \text{ W}$, $V_L = 100 \text{ V}$, $R_a = 0.2 \Omega$, $R_{sh} = 100 \Omega$, VOLTAGE DROP PER BRUSH (VDPB) = 1 V, DC SHUNT GENERATOR



We know

$$P_L = V_L I_L \Rightarrow I_L = \frac{P_L}{V_L} = \frac{3000}{100} = 30 \text{ Amp.}$$

Shunt field current


$$I_{sh} = \frac{V_L}{R_{sh}} = \frac{100}{100} = 1 \text{ Amp}$$

Total armature current $I_a = I_{sh} + I_L = 1 + 30 = 31 \text{ Amp. Ans.}$

The generated emf $E_g = I_a R_a + V_L + 2(\text{VDPB}) = 31 \times 0.2 + 100 + 2 \times 1$
 $= 6.2 + 100 + 2 = 108.2 \text{ V Ans.}$

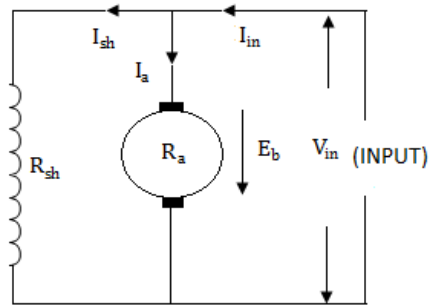Example 9.5 A DC shunt motor runs at 600 rpm taking 60 A from a 240 V supply. Armature resistance is 0.1Ω and field resistance is 120Ω . Find the speed when the current through the armature is 40 A.

Solution: Given $V_{in} = 240 \text{ V}$, $R_a = 0.1 \Omega$, $R_{sh} = 120 \Omega$, DC SHUNT MOTOR



Case 1 When $N_1 = 600 \text{ rpm}$, $I_{in} = 60 \text{ A}$

Shunt field current $I_{sh} = \frac{V_{in}}{R_{sh}} = \frac{240}{120} = 2 \text{ Amp.}$

From the current equation $I_{in} = I_{a1} + I_{sh} \Rightarrow I_{a1} = I_{in} - I_{sh} = 60 - 2 = 58 \text{ A}$

From the voltage equation $V_{in} = I_{a1} R_a + E_{b1} \Rightarrow E_{b1} = V_{in} - I_{a1} R_a = 240 - 58 \times 0.1 = 234.2 \text{ V}$

Case 2 When $N_2 = \text{Find}$, $I_{a2} = 40 \text{ A}$

From the voltage equation $V_{in} = I_{a2} R_a + E_{b2} \Rightarrow E_{b2} = V_{in} - I_{a2} R_a = 240 - 40 \times 0.1 = 236 \text{ V}$

We know

$$N \propto E_b$$

So $N_1 \propto E_{b1}$

and $N_2 \propto E_{b2}$

By dividing, we get

$$\frac{N_1}{N_2} = \frac{E_{b1}}{E_{b2}}$$

$$\frac{600}{N_2} = \frac{234.2}{236} \Rightarrow N_2 = \frac{600 \times 236}{234.2} = 604.6 \text{ rpm}$$

$N_2 = 605 \text{ rpm Ans.}$

Example 9.6 A DC shunt generator running at 1200 rpm supplies a load of 60 kW at 250 V. Find the speed at which it runs as a shunt motor when taking 60 kW from 250 V supply. Take armature resistance is 0.1Ω and field resistance is 50Ω . Brush drop is 2 V per brush.

Solution: Given $R_a = 0.1 \Omega$, $R_{sh} = 50 \Omega$, VOLTAGE DROP PER BRUSH (VDPB) = 2 V

Case 1 DC shunt generator $N_g = 1200 \text{ rpm}$, $P_L = 60 \text{ kW}$, $V_L = 250 \text{ V}$

We know $P_L = V_L I_L \Rightarrow I_L = \frac{P_L}{V_L} = \frac{60000}{250} = 240 \text{ Amp.}$

Shunt field current $I_{sh} = \frac{V_L}{R_{sh}} = \frac{250}{50} = 5 \text{ Amp.}$

From the current equation $I_a = I_{sh} + I_L = 5 + 240 = 245 \text{ Amp.}$

From the voltage equation $E_g = I_a R_a + V_L + 2(\text{VDPB}) = 245 \times 0.1 + 250 + 2 \times 2$
 $= 24.5 + 250 + 4 = 278.5 \text{ V}$

Case 2 DC shunt motor $N_m = \text{Find}$, $P_{in} = 60 \text{ kW}$, $V_{in} = 250 \text{ V}$

We know $P_{in} = V_{in} I_{in} \Rightarrow I_{in} = \frac{P_{in}}{V_{in}} = \frac{60000}{250} = 240 \text{ Amp.}$

Shunt field current $I_{sh} = \frac{V_L}{R_{sh}} = \frac{250}{50} = 5 \text{ Amp.}$

From the current equation $I_{in} = I_{sh} + I_a \Rightarrow I_a = I_{in} - I_{sh} = 240 - 5 = 235 \text{ Amp.}$

From the voltage equation $V_{in} = I_a R_a + E_b + 2(\text{VDPB})$
 $E_b = V_{in} - I_a R_a - 2(\text{VDPB}) = 250 - 235 \times 0.1 - 2 \times 2$
 $= 250 - 23.5 - 4 = 222.5 \text{ V}$

We know $N_g \propto E_g$ and $N_m \propto E_b$

By dividing, we get

$$\frac{N_g}{N_m} = \frac{E_g}{E_b}$$

$$\frac{1200}{N_m} = \frac{278.5}{222.5} \Rightarrow N_m = \frac{1200 \times 222.5}{278.5} = 958.7 \text{ rpm}$$

$$N_m = 959 \text{ rpm Ans.}$$